

PROJECT NAME

TESSERACT

BASED ON

TC Electronic Integrated Preamp

BUILD DIFFICULTY

■■■■□ Intermediate

EFFECT TYPE


Boost/preamp

DOCUMENT VERSION

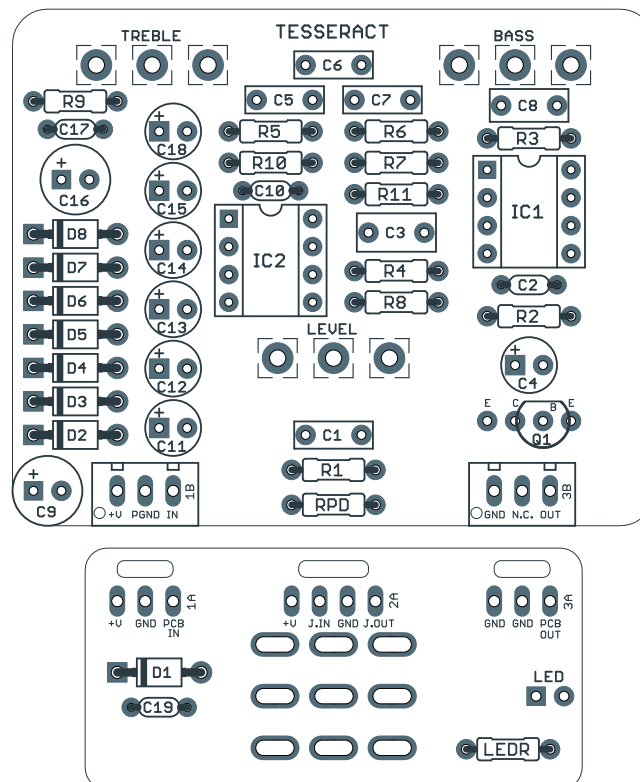1.0.0 (2020-08-28)

PROJECT SUMMARY

A pedal adaptation of the legendary booster and tone shaper famously used by Meshuggah.



Actual size is 2.3" x 1.86" (main board) and 1.78" x 0.86" (bypass board).

TABLE OF CONTENTS

| | | | |
|-----|----------------------|----|--------------------|
| 1 | Project Overview | 7 | Drill Template |
| 2 | Introduction & Usage | 8 | Enclosure Layout |
| 3-4 | Parts List | 9 | Wiring Diagram |
| 5 | Build Notes | 10 | Licensing |
| 6 | Schematic | 10 | Document Revisions |

INTRODUCTION

The Tesseract Boost/Preamp is an adaptation of the TC Electronic Integrated Preamp, a boost & EQ from the late 1970s. The Integrated Pre is so named because it's designed to connect directly to your guitar, which is why the original unit did not have a bypass switch.

The Integrated Preamp gained fame as the secret behind Meshuggah's guitar tone in the 1990s. The boost was perfect for pushing the front of their Mesa/Boogie Dual Rectifiers and they used the EQ to cut the bass for a tighter driven tone.

The original unit could run on as much as 32V using an external supply, or it could operate at the standard 9V using a battery. Since 32V supplies are hard to come by, the Tesseract Boost/Preamp includes an on-board charge pump that quadruples the input voltage (minus a few diode drops), allowing a 32V operation from a standard 9V supply.

The only other modification is the removal of a pop-suppression circuit at the input. This is designed to prevent the loud pop when the input jack is first plugged in. It's essential in the original unit that connected straight to the guitar, since the preamp would reasonably be plugged & unplugged in a live setting and there's no way to mute it. However, in pedal format, the suppression circuit has no function other than to increase the current consumption as it is always bleeding some of the supply voltage to ground. There is no impact to the tone or functionality if it's omitted.

USAGE

The Tesseract has the following controls:

- **Bass** allows boosting or cutting of the 100 Hz band by +/-15dB.
- **Treble** allows boosting or cutting of the 10 KHz band by +/-15dB.
- **Level** controls the overall output of the effect.

PARTS LIST

This parts list is also available in a spreadsheet format which can be imported directly into Mouser for easy parts ordering. Mouser doesn't carry all the parts (most notably potentiometers) so the second tab lists all the non-Mouser parts as well as sources for each.

[View parts list spreadsheet](#) →

| PART | VALUE | TYPE | NOTES |
|------|-------|-------------------------------|---|
| R1 | 4k7 | Metal film resistor, 1/4W | |
| R2 | 6M8 | Metal film resistor, 1/4W | |
| R3 | 100k | Metal film resistor, 1/4W | |
| R4 | 220k | Metal film resistor, 1/4W | |
| R5 | 470R | Metal film resistor, 1/4W | |
| R6 | 4k7 | Metal film resistor, 1/4W | |
| R7 | 8k2 | Metal film resistor, 1/4W | |
| R8 | 220R | Metal film resistor, 1/4W | |
| R9 | 10k | Metal film resistor, 1/4W | |
| R10 | 100k | Metal film resistor, 1/4W | |
| R11 | 1M | Metal film resistor, 1/4W | R11 is shown as 820k in one of the two known factory schematics. |
| RPD | 2M2 | Metal film resistor, 1/4W | Input pulldown resistor. |
| LEDR | 4k7 | Metal film resistor, 1/4W | LED current-limiting resistor. Adjust value to change LED brightness. |
| C1 | 47n | Film capacitor, 7.2 x 2.5mm | |
| C2 | 100pF | MLCC capacitor, NP0/COG | |
| C3 | 1uF | Film capacitor, 7.2 x 3.5mm | |
| C4 | 4.7uF | Electrolytic capacitor, 4mm | |
| C5 | 4n7 | Film capacitor, 7.2 x 2.5mm | |
| C6 | 47n | Film capacitor, 7.2 x 2.5mm | |
| C7 | 22n | Film capacitor, 7.2 x 2.5mm | |
| C8 | 220n | Film capacitor, 7.2 x 2.5mm | |
| C9 | 100uF | Electrolytic capacitor, 6.3mm | |
| C10 | 470n | MLCC capacitor, X7R | |
| C11 | 10uF | Electrolytic capacitor, 5mm | Must be rated for at least 50V. |
| C12 | 10uF | Electrolytic capacitor, 5mm | Must be rated for at least 50V. |
| C13 | 10uF | Electrolytic capacitor, 5mm | Must be rated for at least 50V. |
| C14 | 10uF | Electrolytic capacitor, 5mm | Must be rated for at least 50V. |
| C15 | 10uF | Electrolytic capacitor, 5mm | Must be rated for at least 50V. |
| C16 | 47uF | Electrolytic capacitor, 6.3mm | Must be rated for at least 50V. |
| C17 | 470n | MLCC capacitor, X7R | |

PARTS LIST, CONT.

| PART | VALUE | TYPE | NOTES |
|--------|--------------|--------------------------------|---|
| C18 | 10uF | Electrolytic capacitor, 5mm | Must be rated for at least 50V. |
| C19 | 100n | MLCC capacitor, X7R | |
| D1 | 1N5817 | Schottky diode, DO-41 | |
| D2 | 1N4742A | Zener diode, 12V, DO-41 | |
| D3 | 1N5817 | Schottky diode, DO-41 | |
| D4 | 1N5817 | Schottky diode, DO-41 | |
| D5 | 1N5817 | Schottky diode, DO-41 | |
| D6 | 1N5817 | Schottky diode, DO-41 | |
| D7 | 1N5817 | Schottky diode, DO-41 | |
| D8 | 1N5817 | Schottky diode, DO-41 | |
| Q1 | 2N5088 | BJT transistor, NPN, TO-92 | Original uses BC548C, which will need to be rotated 180 degrees if used since the pinout is mirrored. |
| IC1 | LM741 | Operational amplifier, DIP8 | Factory schematic also specifies TL071 and LF356, but all photos of real units show LM741. |
| IC1-S | DIP-8 socket | IC socket, DIP-8 | |
| IC2 | LT1054CP | Charge pump, DIP8 | |
| IC2-S | DIP-8 socket | IC socket, DIP-8 | |
| BASS | 50kC | 16mm right-angle PCB mount pot | |
| TREBLE | 50kC | 16mm right-angle PCB mount pot | |
| LEVEL | 50kA | 16mm right-angle PCB mount pot | |
| LED | 5mm | LED, 5mm, red diffused | |
| IN | 1/4" stereo | 1/4" phone jack, closed frame | Switchcraft 112BX or equivalent. |
| OUT | 1/4" mono | 1/4" phone jack, closed frame | Switchcraft 111X or equivalent. |
| DC | 2.1mm | DC jack, 2.1mm panel mount | Mouser 163-4302-E or equivalent. |
| BATT | Battery snap | 9V battery snap | Optional. Use the soft plastic type—the hard-shell type will not fit. |
| FSW | 3PDT | Stomp switch, 3PDT | |
| ENC | 125B | Enclosure, die-cast aluminum | Can also use a Hammond 1590N1. |

BUILD NOTES

Q1 transistor

The original unit uses a BC548C for the Q1 transistor, which is a high-gain BJT that is nearly identical to the more common 2N5088. The BC548 is still available. However, Aion FX projects use a universal transistor pad layout, and the outline is for the USA E-B-C pinout (2N5088, 2N3904, etc.). If using an original BC548, note that due to the European C-B-E convention, it will need to be rotated 180 degrees from the outline on the PCB.

R11 resistor

The R11 resistor is shown as 820k in one early factory schematic. The other factory schematic shows 1M. Using 820k it would have the effect of lowering the bias voltage slightly, but in general it shouldn't impact the sound. It's not known which resistor was used more often in production units, but the 1M value appears to be the later version, so it's likely they made the change from 820k for a reason.

Charge pump operation

The Tesseract uses a charge pump to generate approximately +32V from a standard 9V supply. This is done by using a charge pump IC in a configuration that quadruples the input voltage. (In actuality, it's a little less than quadruple due to the forward-voltage loss from the diodes.)

The Integrated Preamp user manual says it can be powered by "up to" 32V. The circuit can handle a fair amount higher than this, so it's not a hard limit—it was likely just a standard power supply interval at the time. It could also be powered by a standard 9V battery, so there were a lot of options.

If you want the Tesseract to run on less than 32V, you can jumper some of the diodes and omit some capacitors to either omit the voltage multiplication entirely or else use it as a doubler or tripler instead:

- For 9V operation, omit **IC1**, jumper **D3-D8** and omit **C11-C15**.
- For 18V operation (voltage doubler), jumper **D5-D8** and omit **C13-C15**.
- For 27V operation (voltage tripler), jumper **D7-D8** and omit **C15**.



Note that while the circuit will probably work with a standard TC1044SCPA, the LT1054 is recommended for its improved specifications and efficiency. It's doing a lot more work in this application than a standard voltage doubler or inverter.

Voltage vs. gain

A word about the voltage: since the gain of the IC1 op-amp is fixed, higher voltage doesn't mean more available volume. Instead, what it means is that it has more headroom. At 32V supply, the circuit can take a much higher input signal (2.5V peak-to-peak) and boost it to 25V p-p without clipping. Compare this to 9V operation, where it can only handle a 0.7V input signal and boost it to 7V.

Since passive electric guitar signals are only around 0.3Vp-p, this won't make a huge practical difference. If you're using it to boost an already boosted signal, though, this circuit can do a much better job than most others.

SCHEMATIC

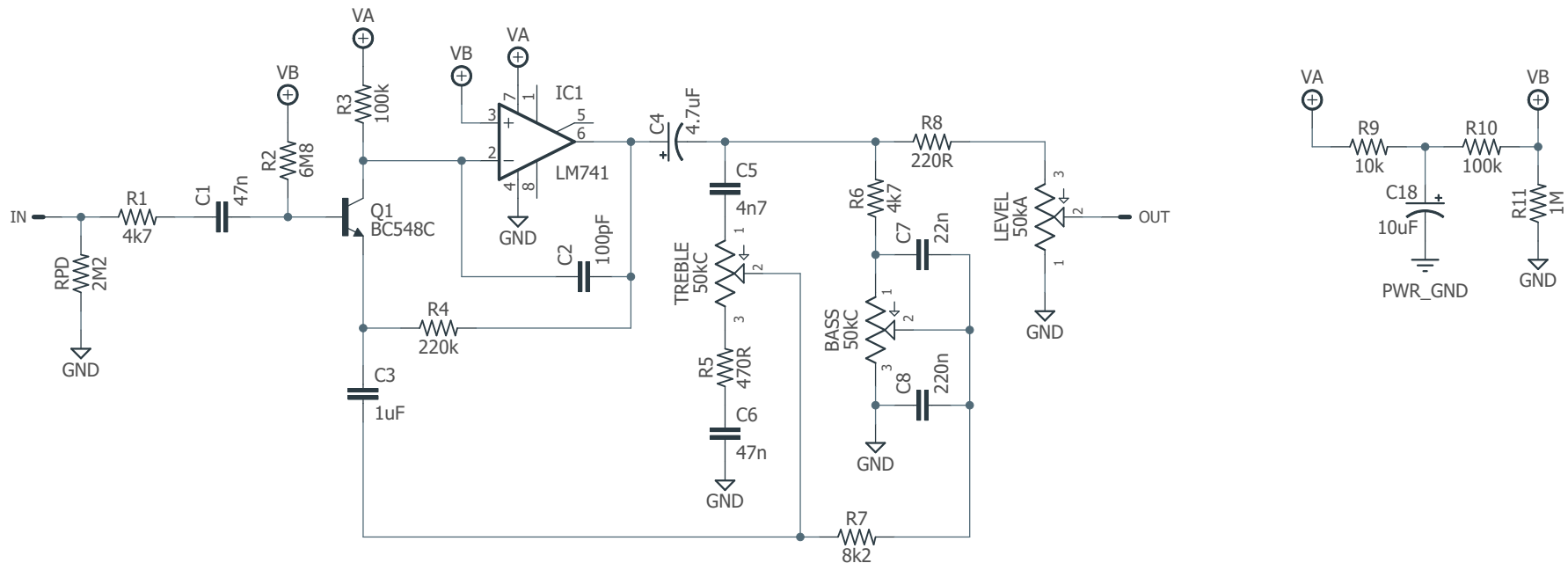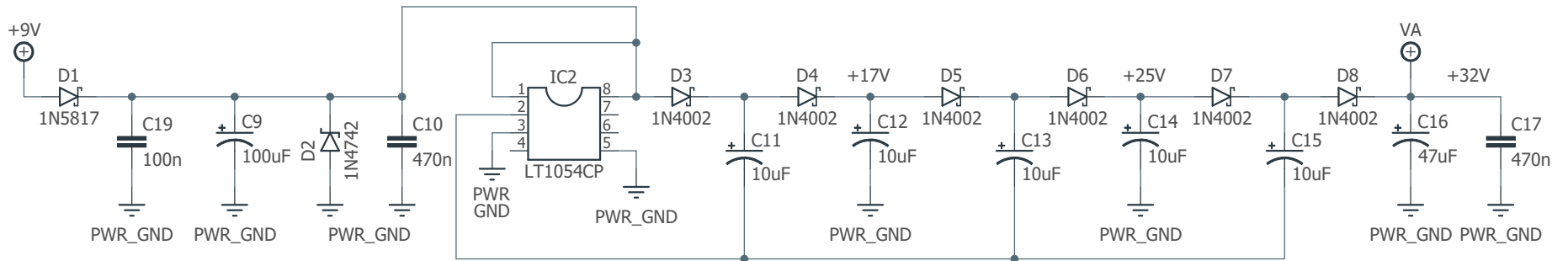


DRILL TEMPLATE

Cut out this drill template, fold the edges and tape it to the enclosure. Before drilling, it's recommended to first use a center punch for each of the holes to help guide the drill bit.

Ensure that this template is printed at 100% or "Actual Size". You can double-check this by measuring the scale on the printed page.


Top jack layout assumes the use of closed-frame jacks like the [Switchcraft 111X](#). If you'd rather use open-frame jacks, please refer to the Open-Frame Jack Drill Template for the top side.

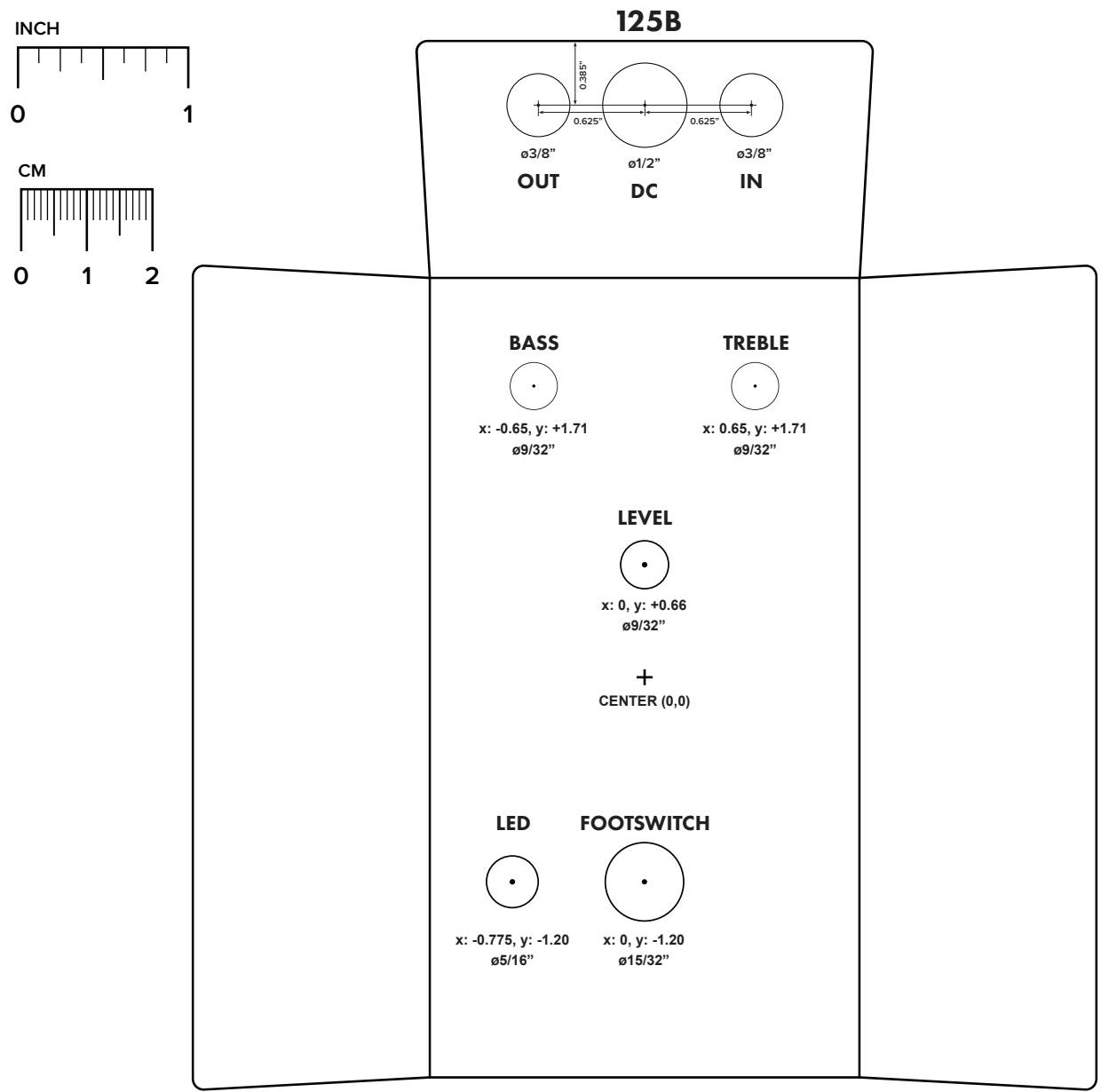LED hole drill size assumes the use of a [5mm LED bezel](#), available from several parts suppliers. Adjust size accordingly if using something different, such as a 3mm bezel, a plastic bezel, or just a plain LED.




ENCLOSURE LAYOUT

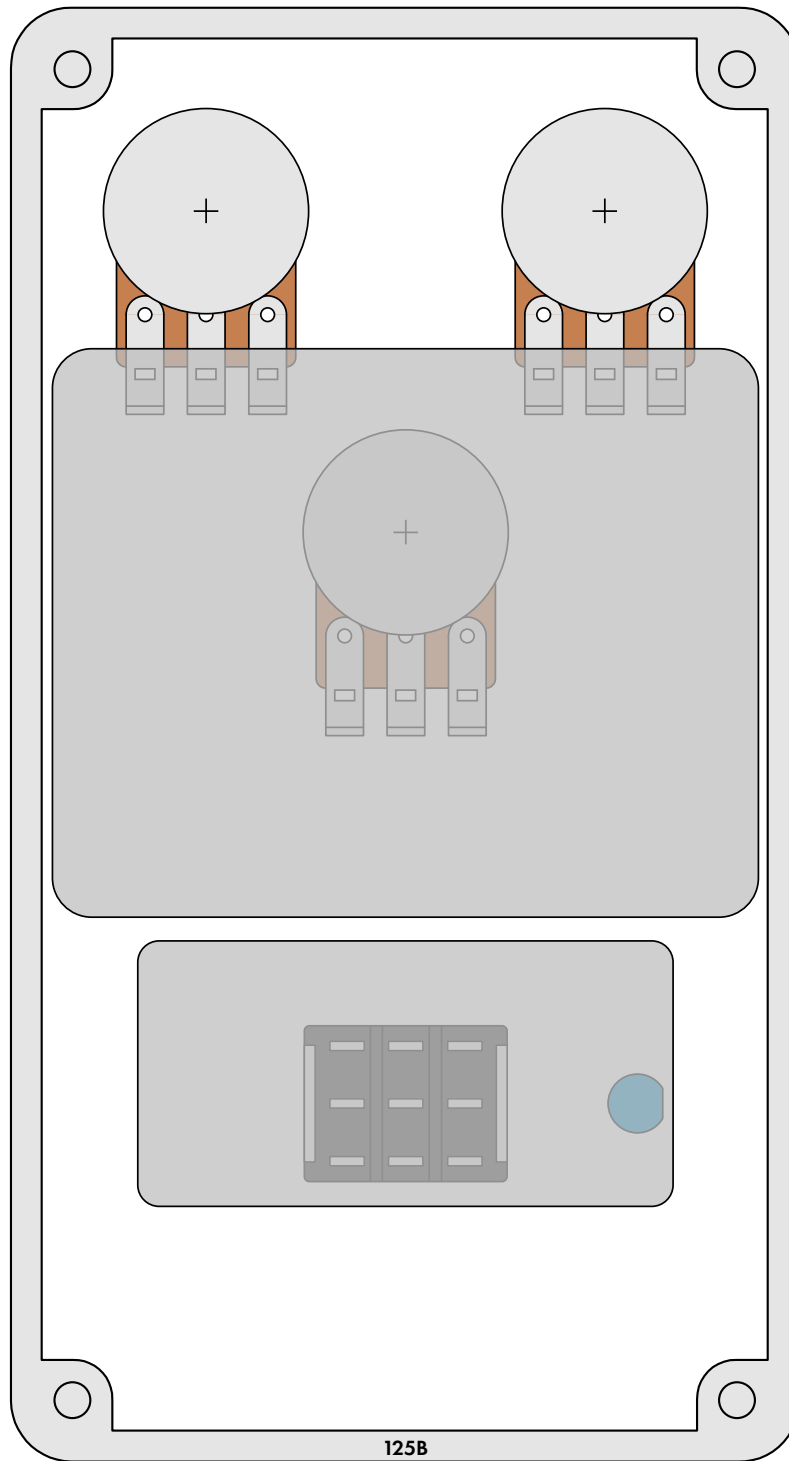Enclosure is shown without jacks. See next page for jack layout and wiring.



WIRING DIAGRAM

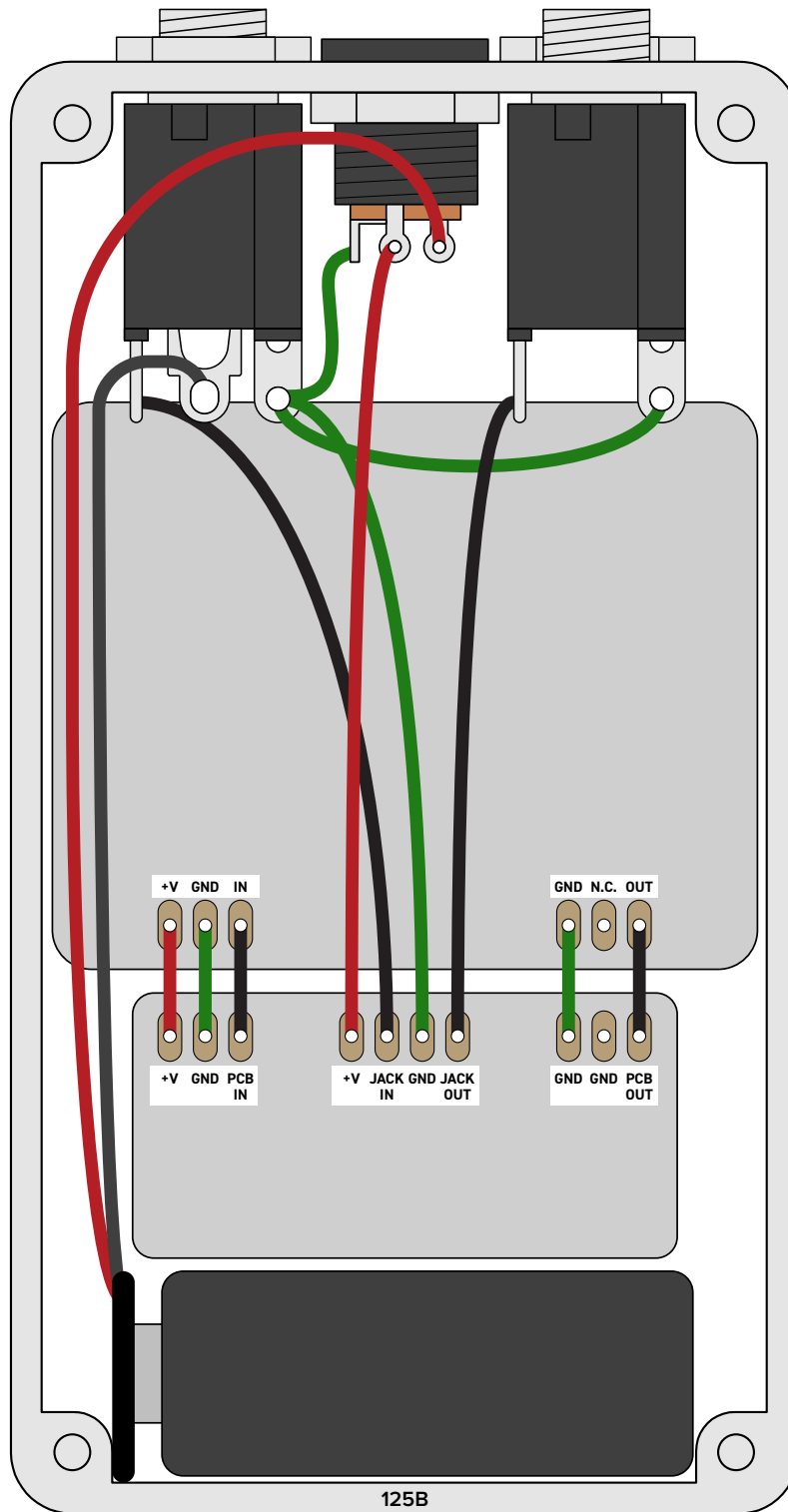

*Shown with optional 9V battery. If battery is omitted, both jacks can be mono rather than one being stereo.
Leave the far-right lug of the DC jack unconnected.*

LICENSE & USAGE

No direct support is offered for these projects beyond the provided documentation. It's assumed that you have at least some experience building pedals before starting one of these. Replacements and refunds cannot be offered unless it can be shown that the circuit or documentation are in error.

All of these circuits have been tested in good faith in their base configurations. However, not all the modifications or variations have necessarily been tested. These are offered only as suggestions based on the experience and opinions of others.

Projects may be used for commercial endeavors in any quantity unless specifically noted. No attribution is necessary, though a link back is always greatly appreciated. The only usage restrictions are that **(1) you cannot resell the PCB as part of a kit without prior arrangement, and (2) you cannot "goop" the circuit, scratch off the screenprint, or otherwise obfuscate the circuit to disguise its source.** (In other words: you don't have to go out of your way to advertise the fact that you use these PCBs, but please don't go out of your way to hide it. The guitar effects industry needs more transparency, not less!)

DOCUMENT REVISIONS

1.0.0 (2020-08-28)

Initial release.